

LOGIC DIAGRAMS

Boolean Expression:

Diagram 1:

$$(x + y')z + \bar{x}y\bar{z}$$

Diagram 2:

$$\overline{(ac + \bar{a}\bar{c}) + \bar{b}} \cdot \overline{(b+d) \cdot \bar{b}}$$

Diagram 3:

$$\left\{ \overline{\overline{bc}} \oplus (\bar{b}c \cdot b) \right\} + \bar{a} \cdot (\bar{b}c \cdot b)$$

Diagram 4:

$$F = A \cdot B + (A \oplus B) \cdot C$$

$$G = (A \oplus B) \oplus C$$

Diagram 5:

$$F_1 = [\overline{(B+C) \cdot A + (A+\bar{B}) + C}]$$

$$F_2 = [\overline{(A+\bar{B}) + C \cdot (\bar{C} \oplus D)}]$$

$$F_3 = [\overline{(A+\bar{B}) \oplus D}]$$

SIMPLIFIED EXPRESSIONS

Diagram 1:

$$(x + \bar{y})z + \bar{x}yz \\ xz + yz + \bar{x}yz$$

Diagram 2:

$$(ac + \bar{a}\bar{c}) + \bar{b} \cdot (b+d) \cdot \bar{b}$$

$$(\bar{a}c + \bar{a}\bar{c}) \cdot \bar{b} \cdot (\bar{b}+d) + \bar{b}$$

$$(\bar{a} + \bar{c}) \cdot \bar{b} \cdot (\bar{b}+d) + \bar{b}$$

$$(a + c) \cdot b \cdot [(\bar{b} \cdot \bar{d}) + b]$$

$$[\bar{a}bc + ab\bar{c}] \cdot [b + \bar{b}\bar{d}]$$

$$\bar{a}b \cdot bc + \bar{a}b \bar{b}\bar{d}c + ab\bar{c}b + ab\bar{b}\bar{c}\bar{d}$$

$$\therefore c \cdot \bar{c} = 0 \text{ or } b \cdot b = b$$

$$\bar{a}bc + ab\bar{c}$$

$$b(\bar{a}c + a\bar{c}) \text{ or } b(a + c)$$

Diagram 3:

$$\{\bar{B}\bar{C} + \bar{B}\bar{C} \oplus (\bar{B}\bar{C} \cdot B)\} + \bar{A} \cdot \bar{B}\bar{C} \cdot \bar{B}$$

$$\{\bar{B}\bar{C} + \bar{B}\bar{C} \oplus (\bar{B} + \bar{C}) \cdot B\} + \{\bar{A} + (\bar{B}\bar{C} \cdot B)\}$$

$$\{\bar{B}\bar{C} + \bar{B}\bar{C} \oplus \bar{B}\bar{C}\} + \{\bar{A} + (\bar{B}\bar{C} + \bar{B})\} \rightarrow \bar{B} + \bar{B}\bar{C} = \bar{B}$$

$$\{\bar{B}\bar{C} + \bar{B}\bar{C} + \bar{B}\bar{C} \cdot (\bar{B}\bar{C})\} + \{\bar{A} + \bar{B} + \bar{C}\}$$

$$\{\bar{B} + \bar{C}\} \cdot \bar{B}\bar{C} + \bar{B}\bar{C} \cdot (\bar{B} + \bar{C}) + (\bar{A} + \bar{B} + \bar{C})$$

$$\bar{B}\bar{C} + \bar{B}\bar{C} + \bar{A} + \bar{B} + \bar{C} \quad \therefore \bar{C} + \bar{C} = 1$$

$$\bar{B} + \bar{B} + \bar{A} + \bar{C} \\ 1 + \bar{A} + \bar{C} = 1$$

Diagram 4:

For F:

$$AB + (\bar{A}B + A\bar{B}) \cdot C$$

$$AB + \bar{A}BC + A\bar{B}C$$

$$A(B + \bar{B}C) + \bar{A}BC$$

$$A(B + C) + \bar{A}BC$$

$$AB + AC + \bar{A}BC$$

$$AB + C(A + \bar{A}B)$$

$$AB + C(A + B)$$

$$F = AB + AC + BC.$$

For G:

$$(\bar{A}B + A\bar{B})C + \bar{C}(\bar{A}B + A\bar{B})$$

$$(\bar{A}B \cdot A\bar{B}) \cdot C + \bar{A}BC + A\bar{B}C$$

$$\{(A + \bar{B}) \cdot (\bar{A} + B)\}C + \bar{A}BC + A\bar{B}C$$

$$(AB + \bar{A}\bar{B})C + \bar{A}BC + A\bar{B}C$$

$$ABC + \bar{A}BC + \bar{A}BC + A\bar{B}C$$

$$A(BC + \bar{B}C) + \bar{A}(BC + \bar{B}C)$$

$$G = A \cdot (B \oplus C) + \bar{A}(B \oplus C)$$

Diagram 5:

For F_1 :

$$(B + C) \cdot A \cdot (A + \bar{B}) + C$$

$$(\bar{B} + C) + \bar{A} \cdot (\bar{A} + \bar{B}) \cdot \bar{C}$$

$$[(\bar{B} \cdot \bar{C}) + \bar{A}] \cdot (\bar{A}B\bar{C})$$

$$\bar{A}B\bar{C} \cdot \bar{B}\bar{C} + \bar{A} \cdot \bar{A}B\bar{C}$$

$$\therefore B \cdot \bar{B} = 0$$

$$F_1 = \bar{A}B\bar{C}$$

For F_2 :

$$\begin{aligned} & \overline{(A + \bar{B}) + C} + (\bar{C}D + \bar{C}\bar{D}) \\ & (\bar{A} + \bar{B}) \cdot \bar{C} + (\bar{C}\bar{D} \cdot \bar{C}\bar{D}) \\ & [(A \cdot B) \cdot \bar{C}] + [(\bar{C} + \bar{D}) \cdot (\bar{C} + \bar{D})] \\ F_2 = & \overline{\bar{A}BC} + (C \oplus D) \end{aligned}$$

For F_3 :

$$\begin{aligned} & \overline{(A + \bar{B}) \cdot D} \cdot \bar{D} \quad (A + \bar{B}) \\ & [\overline{(A + \bar{B})} + \bar{D}] \cdot [D + \overline{(A + \bar{B})}] \\ & [(A + \bar{B}) + \bar{D}] \cdot [D + \bar{A} \cdot \bar{B}] \\ & (A + \bar{B})D + D \cdot \bar{D} + \bar{A}B(A + \bar{B}) + \bar{A}B\bar{D} \\ & AD + \bar{B}D + D + 0 + \bar{A}B\bar{D} \\ F_3 = & AD + \bar{B}D + \bar{A}B\bar{D} \end{aligned}$$

SOP OR POS

Diagram 1:

SOP:

$$\bar{X}\bar{Y}Z + \bar{X}YZ + X\bar{Y}Z + XY\bar{Z}$$

POS:

$$(X+Y+Z)(\bar{X}+\bar{Y}+\bar{Z})(\bar{X}+Y+Z)$$

Diagram 2:

SOP:

$$(\bar{a}bcd) + (\bar{a}bc\bar{d}) + (ab\bar{c}d) + (ab\bar{c}\bar{d})$$

POS:

$$\begin{aligned} & (a+b+c+d)(a+b+c+\bar{d})(a+b+\bar{c}+d) \\ & (a+b+\bar{c}+\bar{d})(\bar{a}+\bar{b}+c+d)(\bar{a}+\bar{b}+c+\bar{d}) \\ & (\bar{a}+b+c+d)(\bar{a}+b+c+\bar{d})(\bar{a}+b+\bar{c}+d) \\ & (\bar{a}+b+\bar{c}+d)(\bar{a}+\bar{b}+\bar{c}+d)(\bar{a}+\bar{b}+\bar{c}+\bar{d}) \end{aligned}$$

Diagram 3:

SOP:

NO SOP

POS:

NO POS

Diagram 4:

SOP For F:

$$\bar{A}BC + A\bar{B}C + AB\bar{C} + ABC$$

SOP For G:

$$\bar{A}\bar{B}C + \bar{A}B\bar{C} + A\bar{B}\bar{C} + ABC$$

POS For F:

$$(A+B+C)(A+B+\bar{C})(A+\bar{B}+C)(\bar{A}+B+\bar{C})$$

POS For G:

$$(A+B+C)(A+\bar{B}+\bar{C})(\bar{A}+B+\bar{C})(\bar{A}+\bar{B}+C)$$

Diagram 5:

SOP For F_1 :

$$(\bar{A}B\bar{C}D) + (\bar{A}B\bar{C}\bar{D})$$

SOP For F_2 :

$$(\bar{A}\bar{B}\bar{C}D) + (\bar{A}\bar{B}\bar{C}\bar{D}) + (\bar{A}B\bar{C}\bar{D}) + (\bar{A}B\bar{C}D)$$
$$(\bar{A}BC\bar{D}) + (A\bar{B}\bar{C}D) + (AB\bar{C}\bar{D}) + (AB\bar{C}D)$$
$$(ABC\bar{D})$$

SOP For F_3 :

$$(\bar{A}\bar{B}\bar{C}D) + (\bar{A}\bar{B}CD) + (\bar{A}B\bar{C}\bar{D}) + (\bar{A}B\bar{C}D) +$$
$$(A\bar{B}\bar{C}D) + (A\bar{B}CD) + (AB\bar{C}D) + (AB\bar{C}\bar{D}) +$$
$$(ABC\bar{D})$$

POS For F_1 :

$$(A+B+C+D) \cdot (A+B+C+\bar{D}) \cdot (A+B+\bar{C}+D) \cdot$$
$$(A+B+\bar{C}+\bar{D}) \cdot (A+\bar{B}+\bar{C}+D) + (A+\bar{B}+\bar{C}+\bar{D})$$
$$(\bar{A}+B+C+D) \cdot (\bar{A}+B+C+\bar{D}) \cdot (\bar{A}+B+\bar{C}+D)$$
$$(A+\bar{B}+\bar{C}+\bar{D}) \cdot (\bar{A}+\bar{B}+C+D) \cdot (\bar{A}+\bar{B}+C+\bar{D})$$
$$(\bar{A}+\bar{B}+\bar{C}+D) \cdot (\bar{A}+\bar{B}+\bar{C}+\bar{D})$$

B

POS for F_2 :

$$(A+B+C+D) \cdot (A+B+\bar{C}+\bar{D}) \cdot (\bar{A}+\bar{B}+\bar{C}+\bar{D})$$
$$(\bar{A}+B+C+D) \cdot (\bar{A}+B+\bar{C}+\bar{D}) \cdot (\bar{A}+\bar{B}+C+D)$$
$$(\bar{A}+\bar{B}+\bar{C}+\bar{D})$$

POS for F_3 :

$$(A+B+C+D) \cdot (A+B+\bar{C}+D)$$

$$(A+\bar{B}+C+\bar{D}) \cdot (A+\bar{B}+\bar{C}+\bar{D})$$

$$(\bar{A}+B+C+D) \cdot (\bar{A}+B+\bar{C}+D)$$

$$(\bar{A}+\bar{B}+C+D)$$

KUTTA TABLES

Diagram. 1:

| A | B | C | AC | $\bar{B}C$ | $\bar{A}YZ$ | $AC + \bar{B}C + \bar{A}BC$ |
|---|---|---|----|------------|-------------|-----------------------------|
| 0 | 0 | 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 0 | 1 | 0 | 1 |
| 0 | 1 | 0 | 0 | 0 | 0 | 0 |
| 0 | 1 | 1 | 0 | 0 | 1 | 1 |
| 1 | 0 | 0 | 0 | 0 | 0 | 0 |
| 1 | 0 | 1 | 1 | 1 | 0 | 1 |
| 1 | 1 | 0 | 0 | 0 | 0 | 0 |
| 1 | 1 | 1 | 1 | 0 | 0 | 1 |

Diagram 2:

| a | b | c | d | $a \oplus c$ | $b(a+c)$ |
|---|---|---|---|--------------|----------|
| 0 | 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 0 | 1 | 0 | 0 |
| 0 | 0 | 1 | 0 | 1 | 0 |
| 0 | 0 | 1 | 1 | 1 | 0 |
| 0 | 1 | 0 | 0 | 0 | 0 |
| 0 | 1 | 0 | 1 | 0 | 0 |
| 0 | 1 | 1 | 0 | 1 | 1 |
| 0 | 1 | 1 | 1 | 1 | 1 |
| 1 | 0 | 0 | 0 | 1 | 0 |
| 1 | 0 | 0 | 1 | 1 | 0 |
| 1 | 0 | 1 | 0 | 0 | 0 |
| 1 | 0 | 1 | 1 | 0 | 0 |
| 1 | 1 | 0 | 0 | 1 | 1 |
| 1 | 1 | 0 | 1 | 1 | 1 |
| 1 | 1 | 1 | 0 | 0 | 0 |
| 1 | 1 | 1 | 1 | 0 | 0 |

Diagram 3

| A | B | C | I |
|---|---|---|---|
| 0 | 0 | 0 | 1 |
| 0 | 0 | 1 | 1 |
| 0 | 1 | 0 | 1 |
| 0 | 1 | 1 | 1 |
| 1 | 0 | 0 | 1 |
| 1 | 0 | 1 | 1 |
| 1 | 1 | 0 | 1 |
| 1 | 1 | 1 | 1 |

Diagram 4:

| A | B | C | F | G |
|---|---|---|---|---|
| 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 0 | 1 |
| 0 | 1 | 0 | 0 | 1 |
| 0 | 1 | 1 | 1 | 0 |
| 1 | 0 | 0 | 0 | 1 |
| 1 | 0 | 1 | 1 | 0 |
| 1 | 1 | 0 | 1 | 0 |
| 1 | 1 | 1 | 1 | 1 |

Diagram 5:

| A | B | C | D | F_1 | F_2 | F_3 |
|---|---|---|---|-------|-------|-------|
| 0 | 0 | 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 0 | 1 | 0 | 1 | 1 |
| 0 | 0 | 1 | 0 | 0 | 1 | 0 |
| 0 | 0 | 1 | 1 | 0 | 0 | 1 |
| 0 | 1 | 0 | 0 | 1 | 1 | 1 |
| 0 | 1 | 0 | 1 | 1 | 1 | 0 |
| 0 | 1 | 1 | 0 | 0 | 1 | 1 |
| 0 | 1 | 1 | 1 | 0 | 0 | 0 |
| 1 | 0 | 0 | 0 | 0 | 0 | 0 |
| 1 | 0 | 0 | 1 | 0 | 1 | 1 |
| 1 | 0 | 1 | 0 | 0 | 1 | 0 |
| 1 | 0 | 1 | 1 | 0 | 0 | 1 |
| 1 | 1 | 0 | 0 | 0 | 0 | 0 |
| 1 | 1 | 1 | 1 | 0 | 1 | 1 |
| 1 | 1 | 1 | 0 | 0 | 1 | 1 |
| 1 | 1 | 1 | 1 | 0 | 0 | 1 |

AND OR NOT DIAGRAMS

Diagram 1:

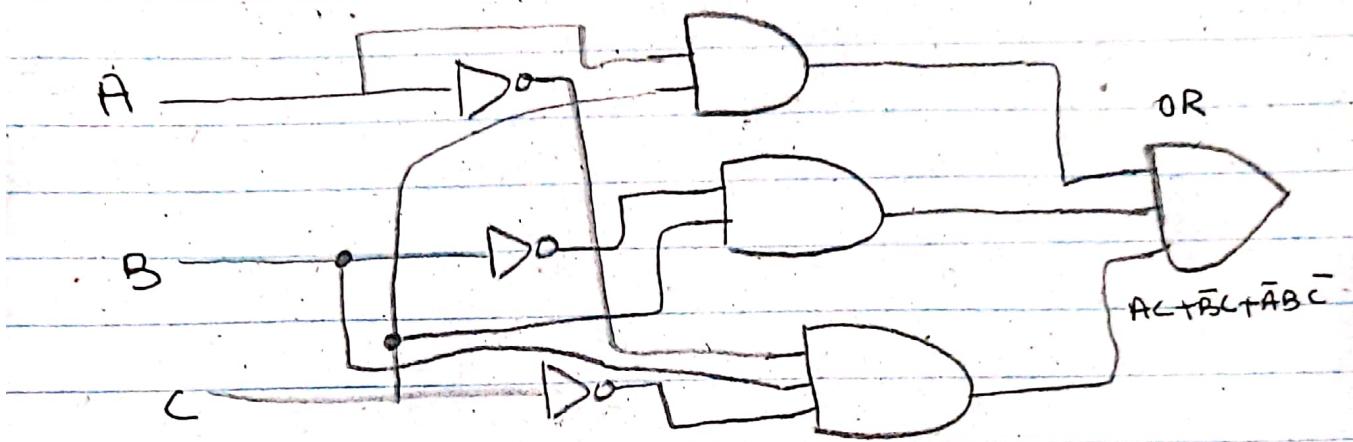


Diagram 2:

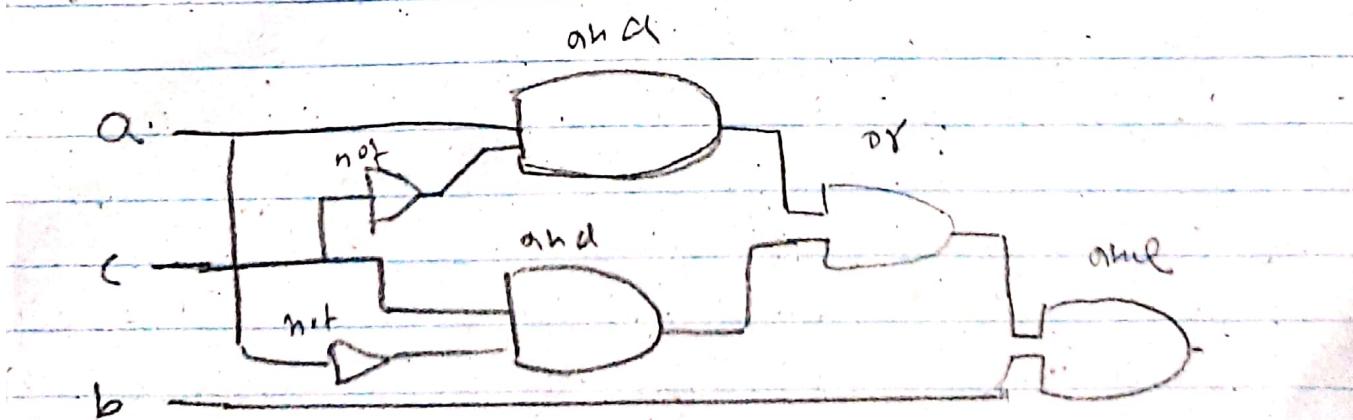


Diagram 3:

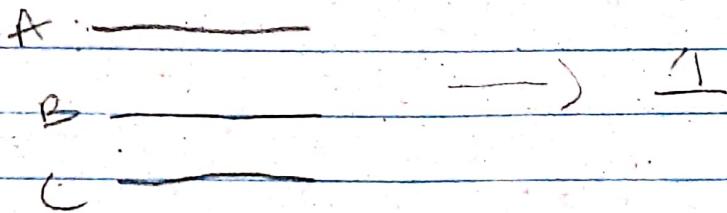


Diagram 4:


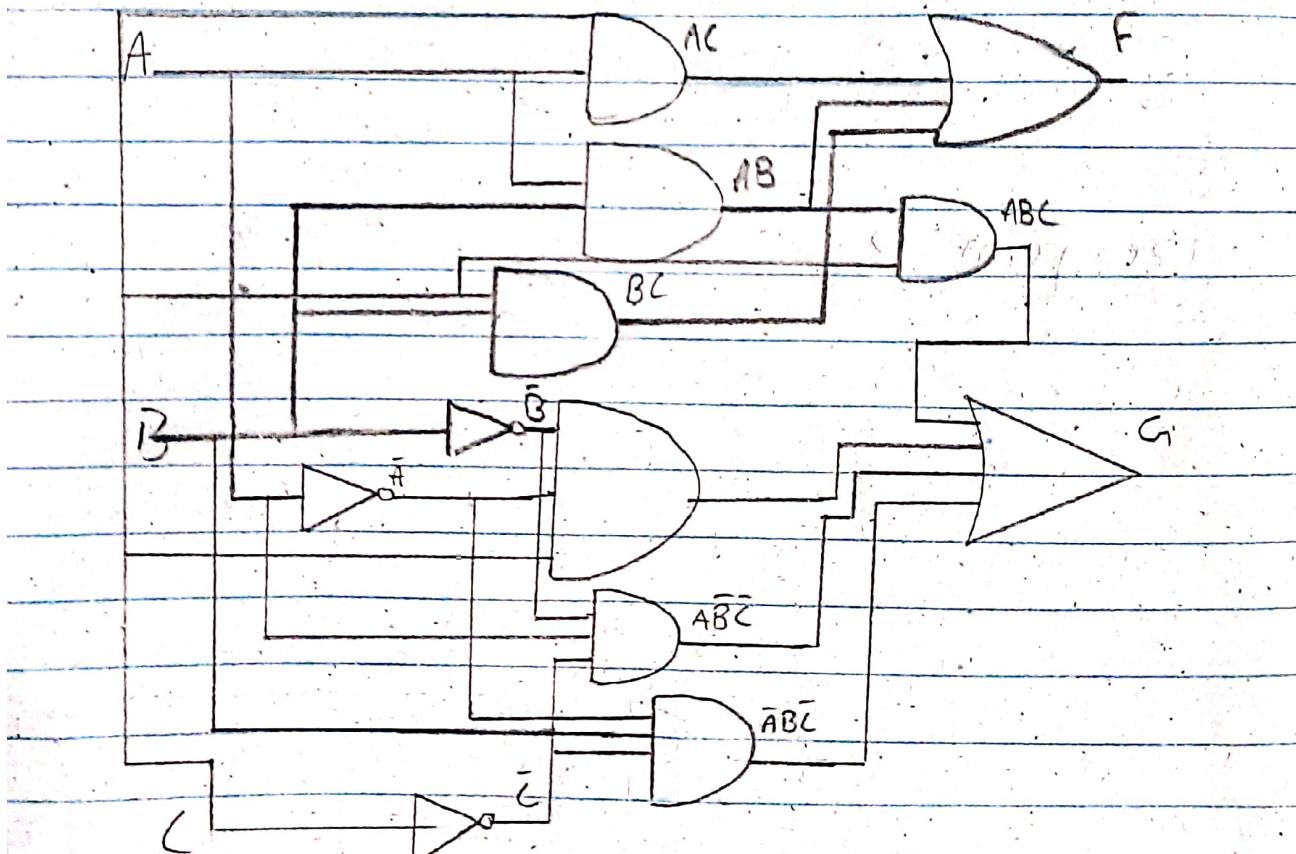


Diagram 5:

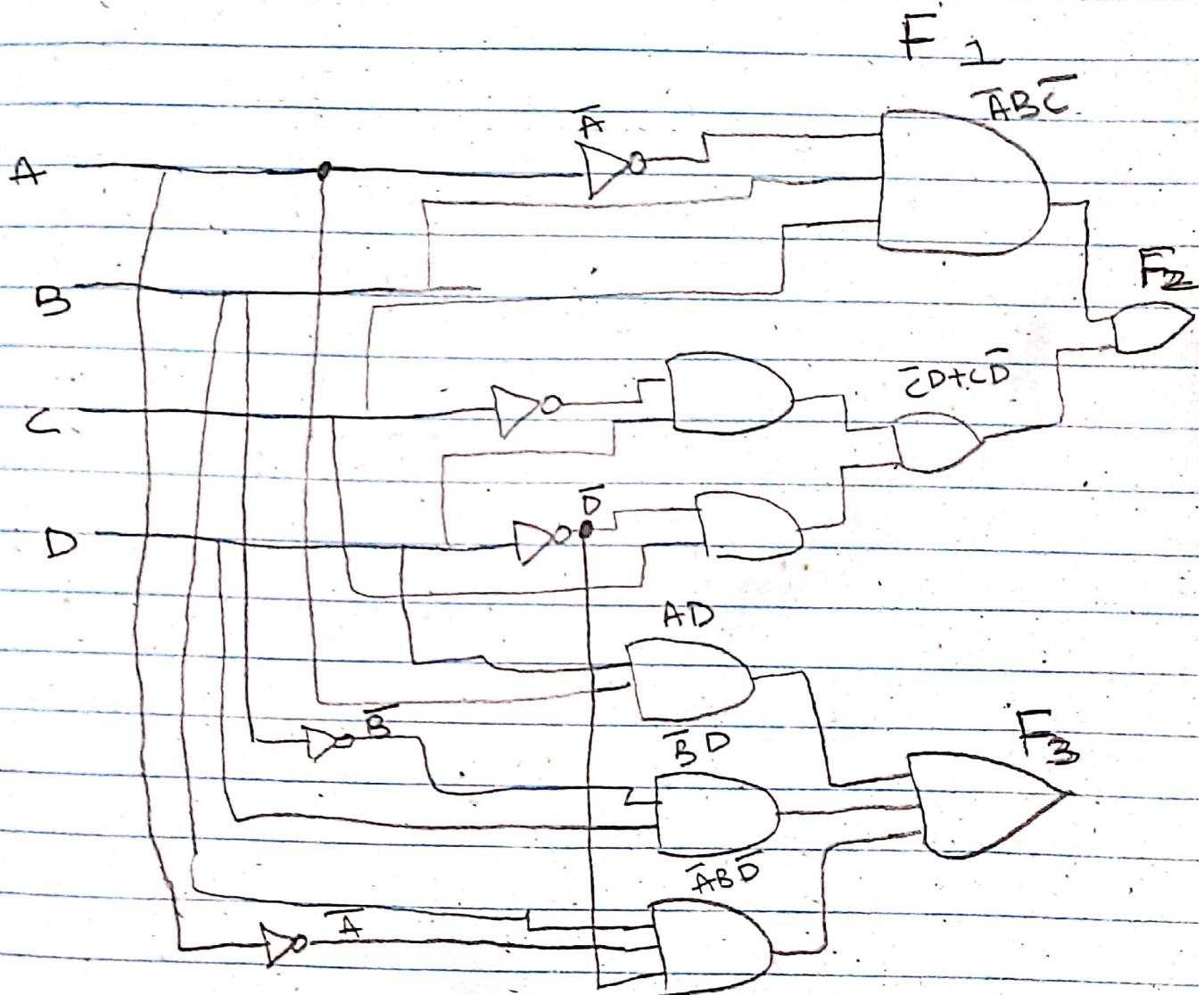

II AND GATE.

Diagram 1:


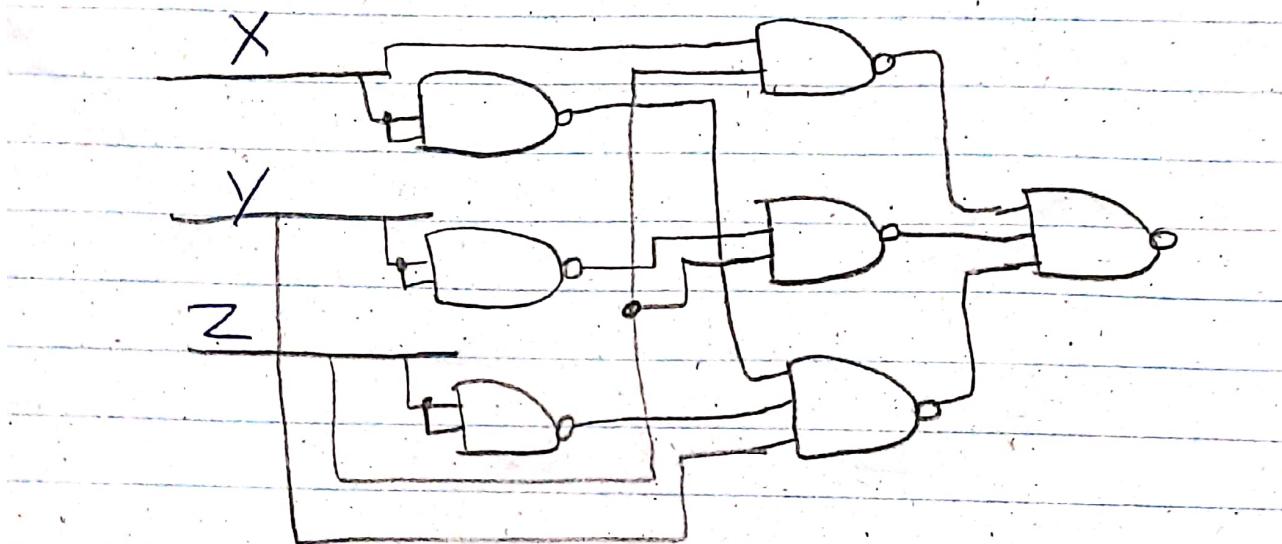


Diagram 2:

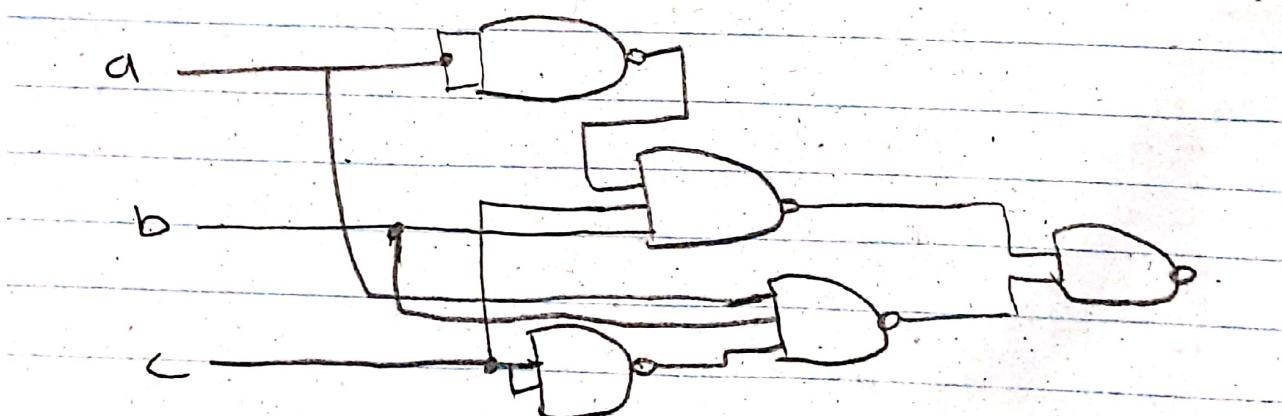

d no effect.

Diagrams 3:

No diagram required because each input give 1.

Diagram 4:


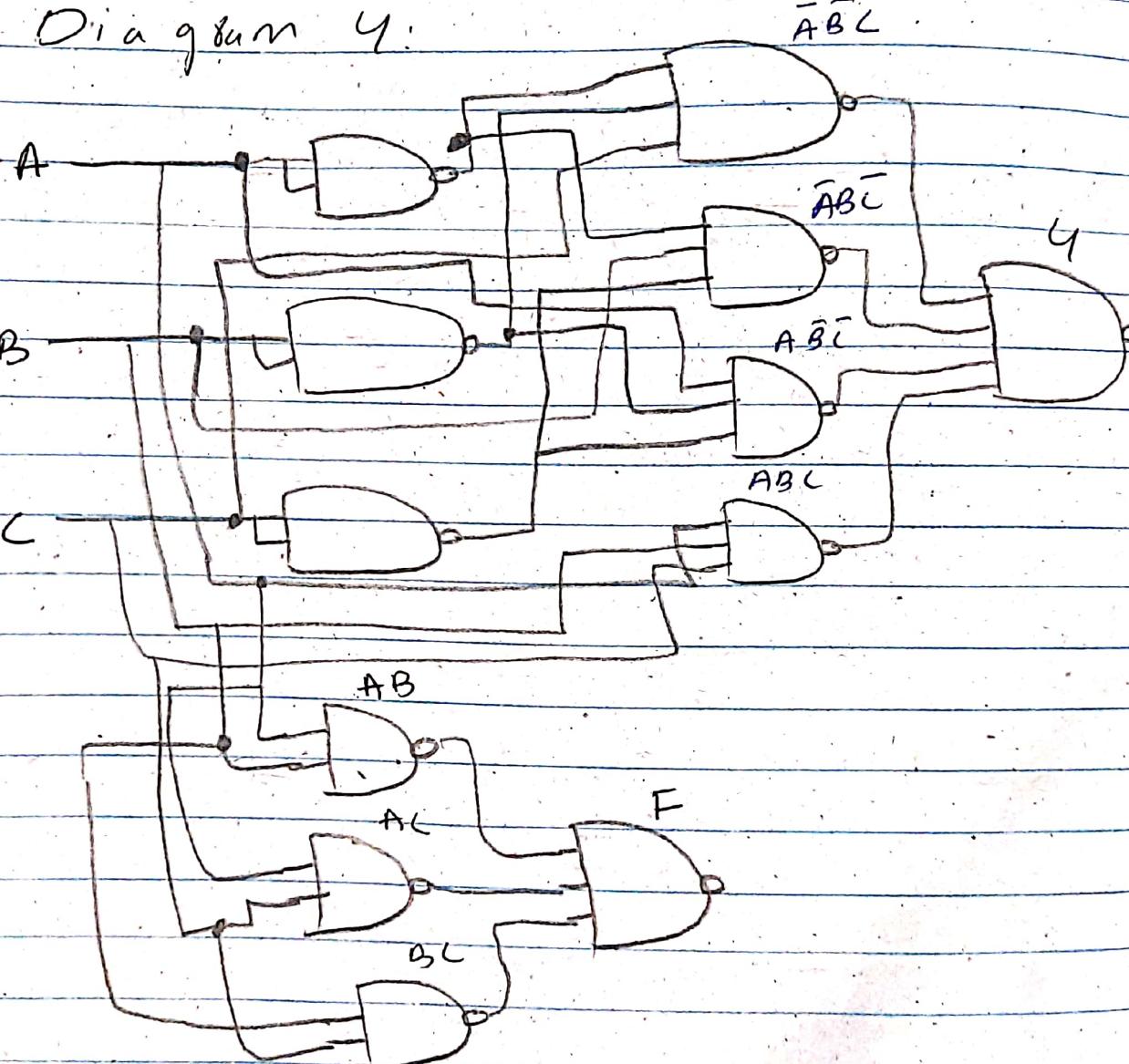


Diagram 5:

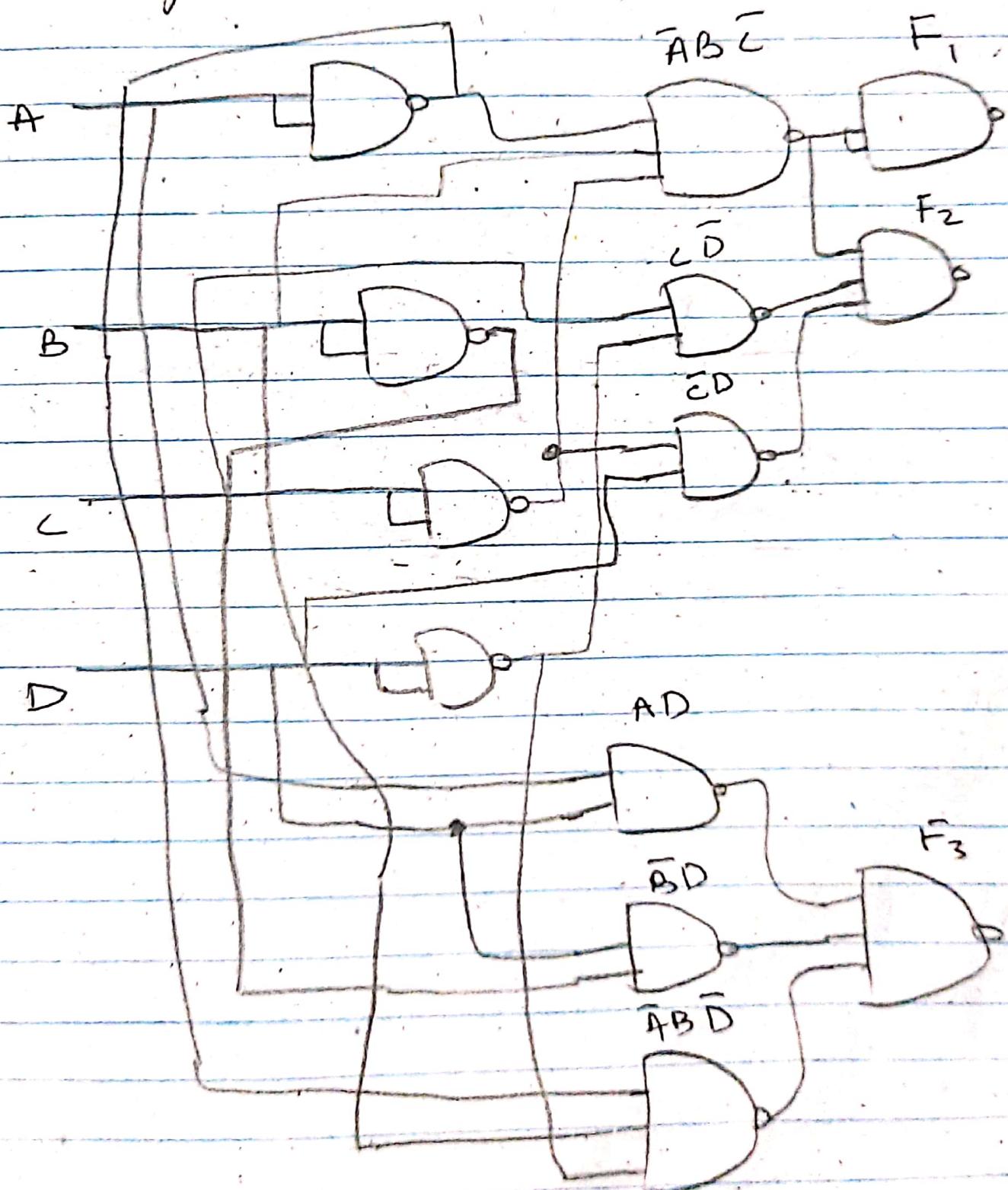

NOR GATE

Diagram 1:


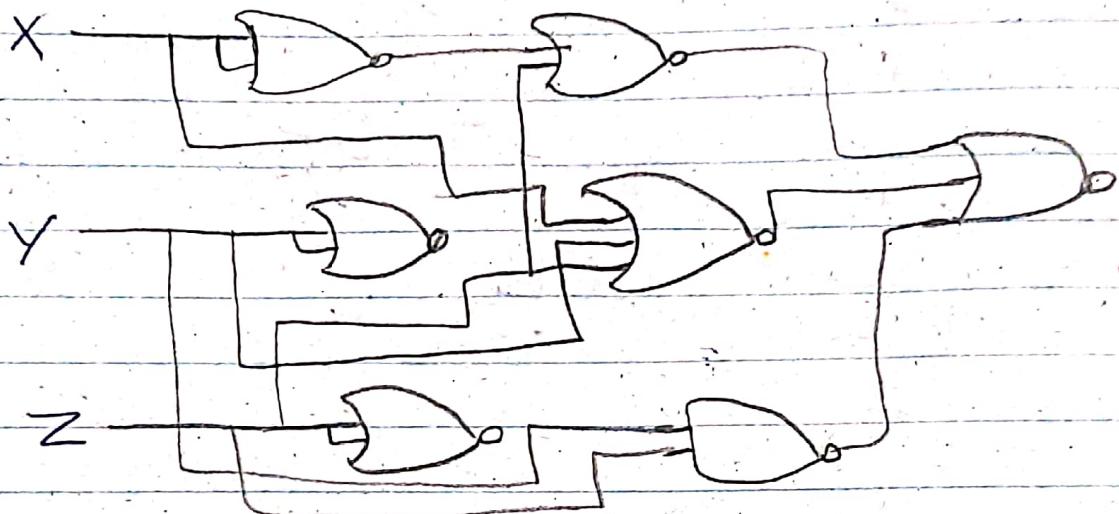


Diagram 2:

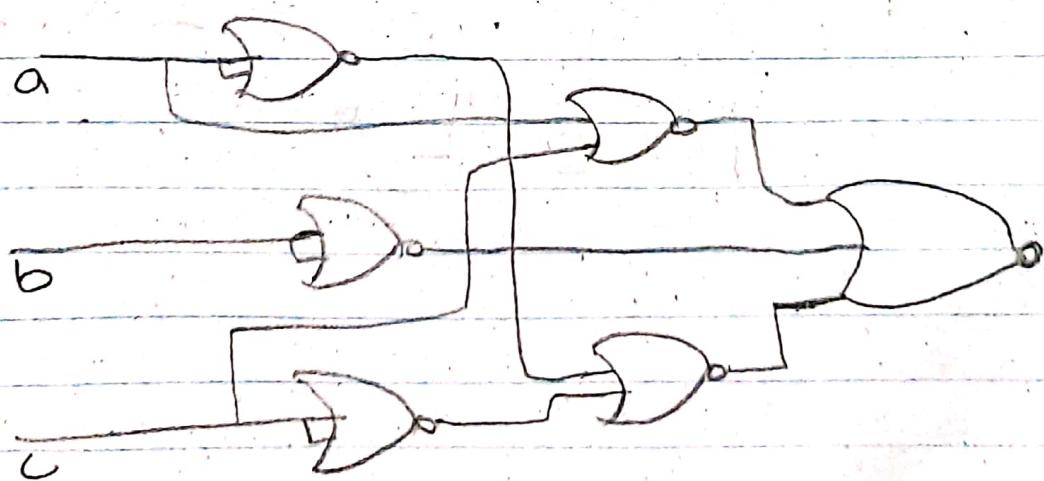

d has no effect

Diagram 3:

An input give 1 so
no diagram required.

Diagram 4:


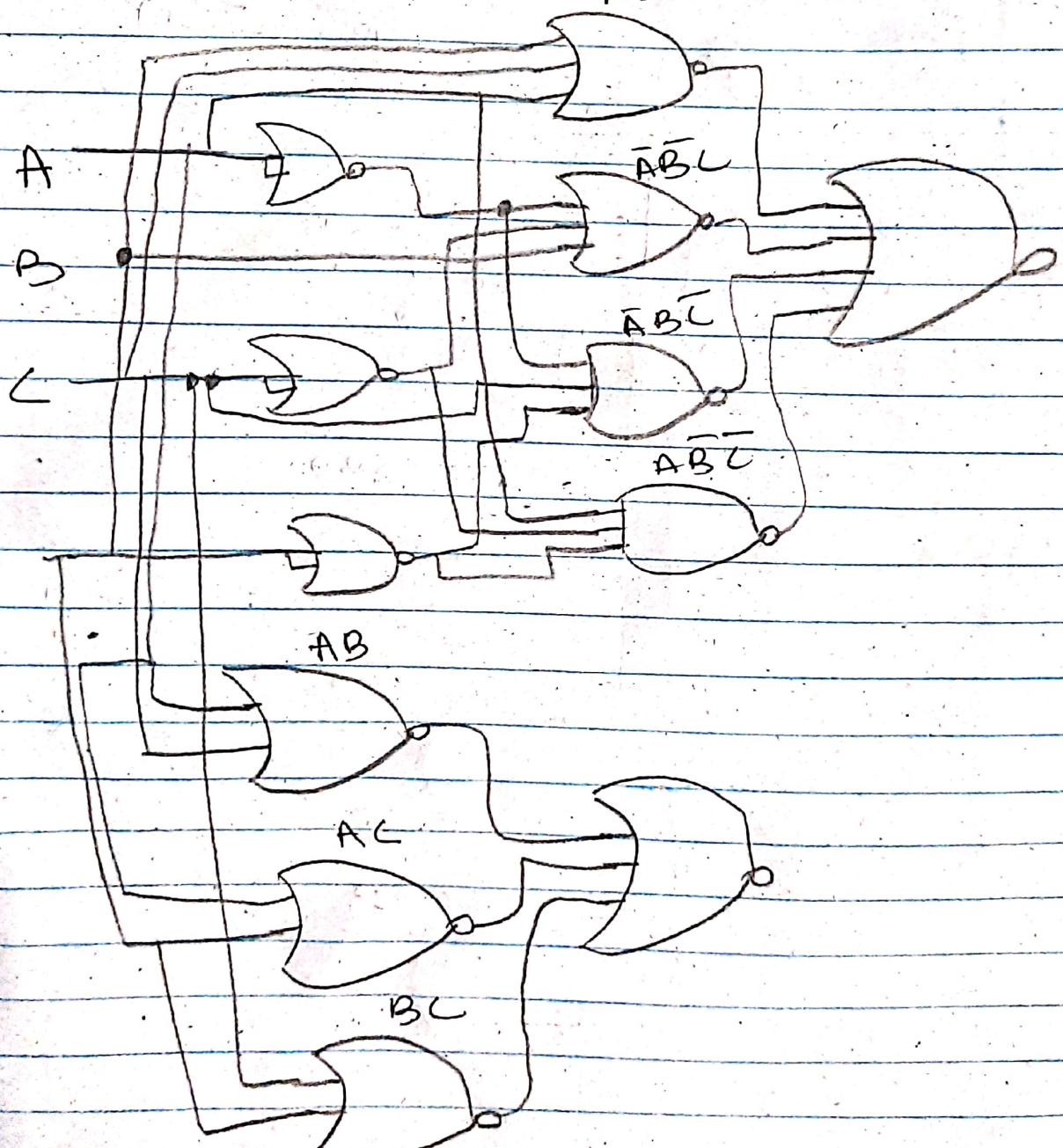


Diagram 5:

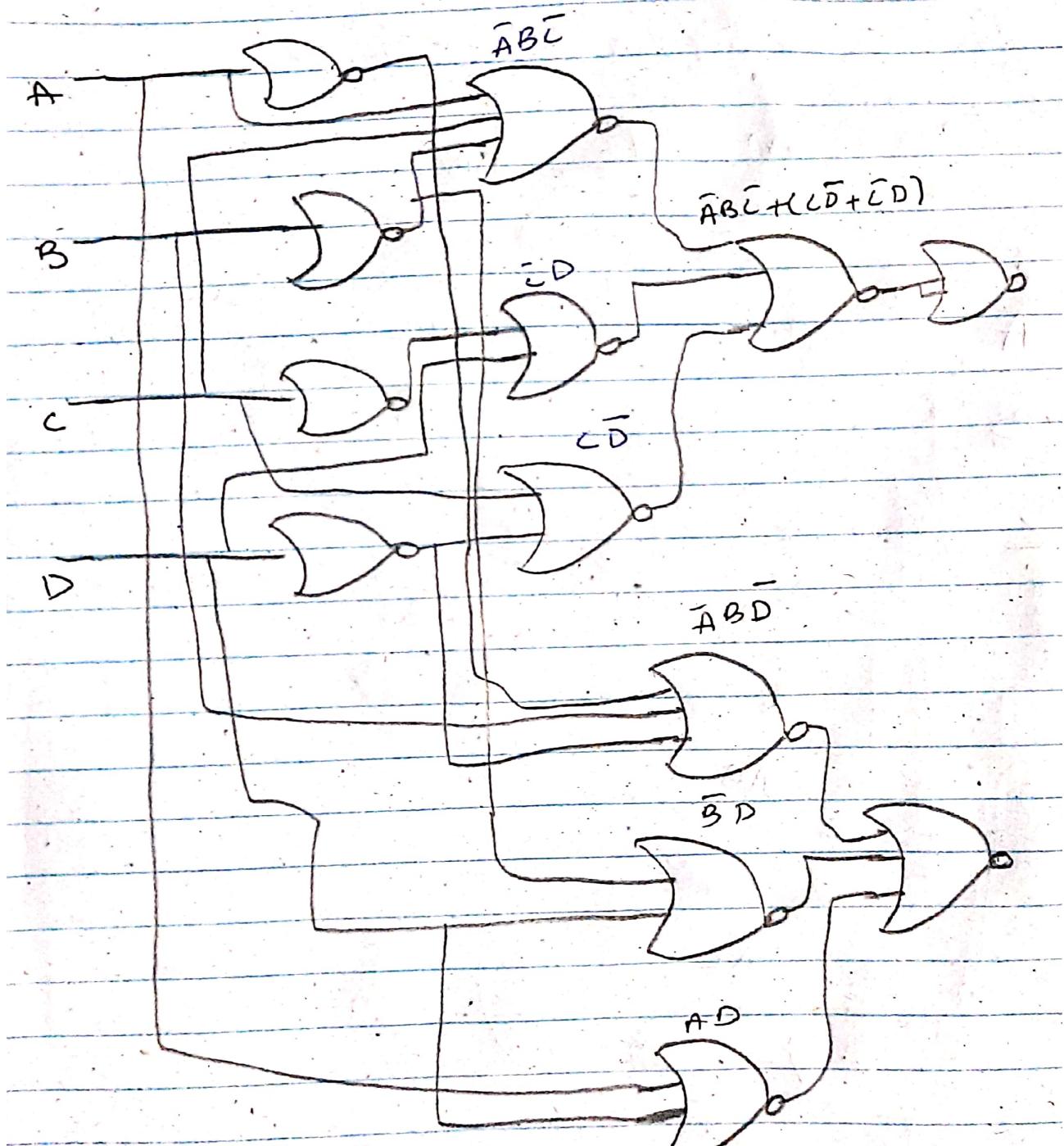

WORD PROBLEMS

1)


| A | B | C | D | X |
|---|---|---|---|---|
| 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 0 | 1 | 0 |
| 0 | 0 | 1 | 0 | 0 |
| 0 | 0 | 1 | 1 | 0 |
| 0 | 1 | 0 | 0 | 0 |
| 0 | 1 | 0 | 1 | 0 |
| 0 | 1 | 1 | 0 | 0 |
| 0 | 1 | 1 | 1 | 1 |
| 1 | 0 | 0 | 0 | 0 |
| 1 | 0 | 0 | 1 | 0 |
| 1 | 0 | 1 | 0 | 0 |
| 1 | 0 | 1 | 1 | 1 |
| 1 | 1 | 0 | 0 | 0 |
| 1 | 1 | 0 | 1 | 1 |
| 1 | 1 | 1 | 0 | 1 |
| 1 | 1 | 1 | 1 | 1 |

| AB | CD | 00 | 01 | 11 | 10 |
|----|----|----|----|----|----|
| 00 | | | | | |
| 01 | | | 1 | | |
| 11 | | 1 | 1 | 1 | 1 |
| 10 | | | | | 1 |

simplified:

$$ABD + ABL + BCD + ALC$$

Diagram:

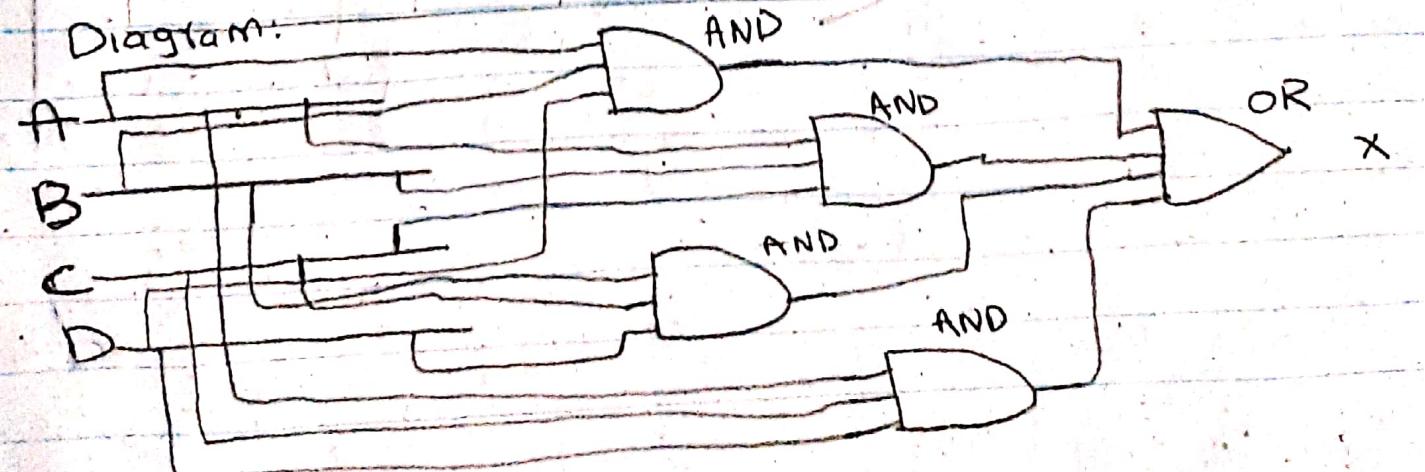

2)


| A | B | C | D | X |
|---|---|---|---|---|
| 0 | 0 | 0 | 0 | 1 |
| 0 | 0 | 0 | 1 | 1 |
| 0 | 0 | 1 | 0 | 1 |
| 0 | 0 | 1 | 1 | 1 |
| 0 | 1 | 0 | 0 | 1 |
| 0 | 1 | 0 | 1 | 1 |
| 0 | 1 | 1 | 0 | 1 |
| 0 | 1 | 1 | 1 | 1 |
| 1 | 0 | 0 | 0 | 1 |
| 1 | 0 | 0 | 1 | 0 |
| 1 | 0 | 1 | 0 | 0 |
| 1 | 0 | 1 | 1 | 0 |
| 1 | 1 | 0 | 0 | 0 |
| 1 | 1 | 0 | 1 | 0 |
| 1 | 1 | 1 | 0 | 0 |
| 1 | 1 | 1 | 1 | 0 |

| CD | AB | 00 | 01 | 11 | 10 |
|----|----|----|----|----|----|
| 00 | 00 | 1 | 1 | 1 | 1 |
| 01 | 01 | 1 | 1 | 1 | 1 |
| 11 | 11 | | | | |
| 10 | 10 | | | | |

simplified:

$$\bar{A} + \bar{B}\bar{C}\bar{D}$$

Diagram:

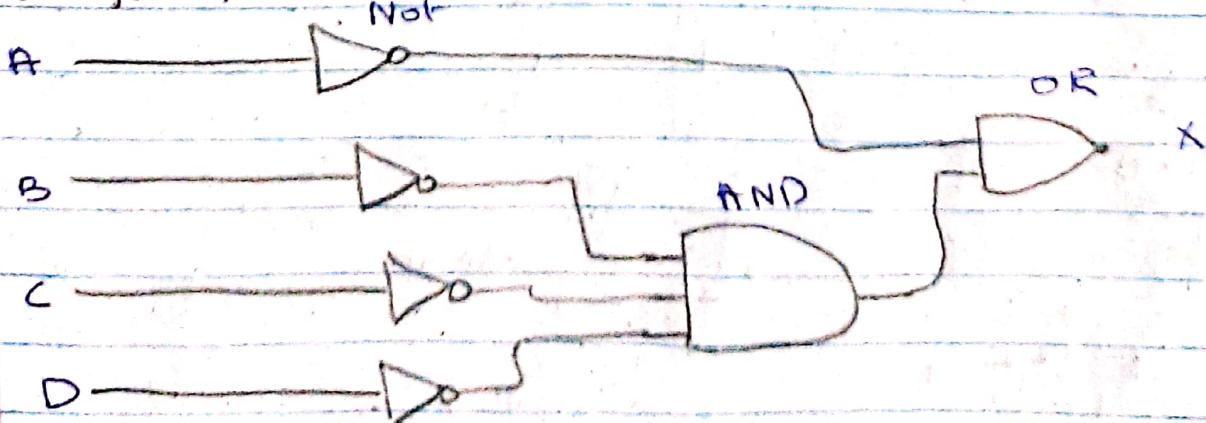

| A | B | C | D | Z | Y | AB | CD |
|---|---|---|---|---|---|----|----|
| 0 | 0 | 0 | 0 | 0 | 1 | 00 | 11 |
| 0 | 0 | 0 | 1 | 1 | 0 | 01 | 11 |
| 0 | 0 | 1 | 0 | 0 | 1 | 11 | 11 |
| 0 | 0 | 1 | 1 | 1 | 0 | 10 | 11 |
| 0 | 1 | 0 | 0 | 0 | 1 | | |
| 0 | 1 | 0 | 1 | 1 | 0 | | |
| 0 | 1 | 1 | 0 | 0 | 1 | | |

Simplified Z:


$$D + \bar{A}BC$$

| A | B | C | D | P | Z | AB | CD |
|---|---|---|---|---|---|----|-------------|
| 0 | 0 | 0 | 0 | 0 | 1 | 00 | 11 |
| 0 | 0 | 1 | 1 | 1 | 0 | 00 | 11 |
| 1 | 0 | 0 | 0 | 0 | 1 | | |
| 1 | 0 | 0 | 1 | 1 | 0 | | |
| 1 | 0 | 1 | 0 | 0 | 1 | AB | 00 01 11 10 |
| 1 | 0 | 1 | 1 | 1 | 0 | 00 | 11 |
| 1 | 1 | 0 | 0 | 0 | 1 | 01 | 11 |
| 1 | 1 | 0 | 1 | 1 | 0 | 11 | 11 |
| 1 | 1 | 1 | 0 | 0 | 1 | 10 | 11 |
| 1 | 1 | 1 | 1 | 1 | 1 | | |

Simplified Y:

$$\bar{A}\bar{C}\bar{D} + \bar{B}\bar{C}\bar{D} + C\bar{D}$$

Diagram:

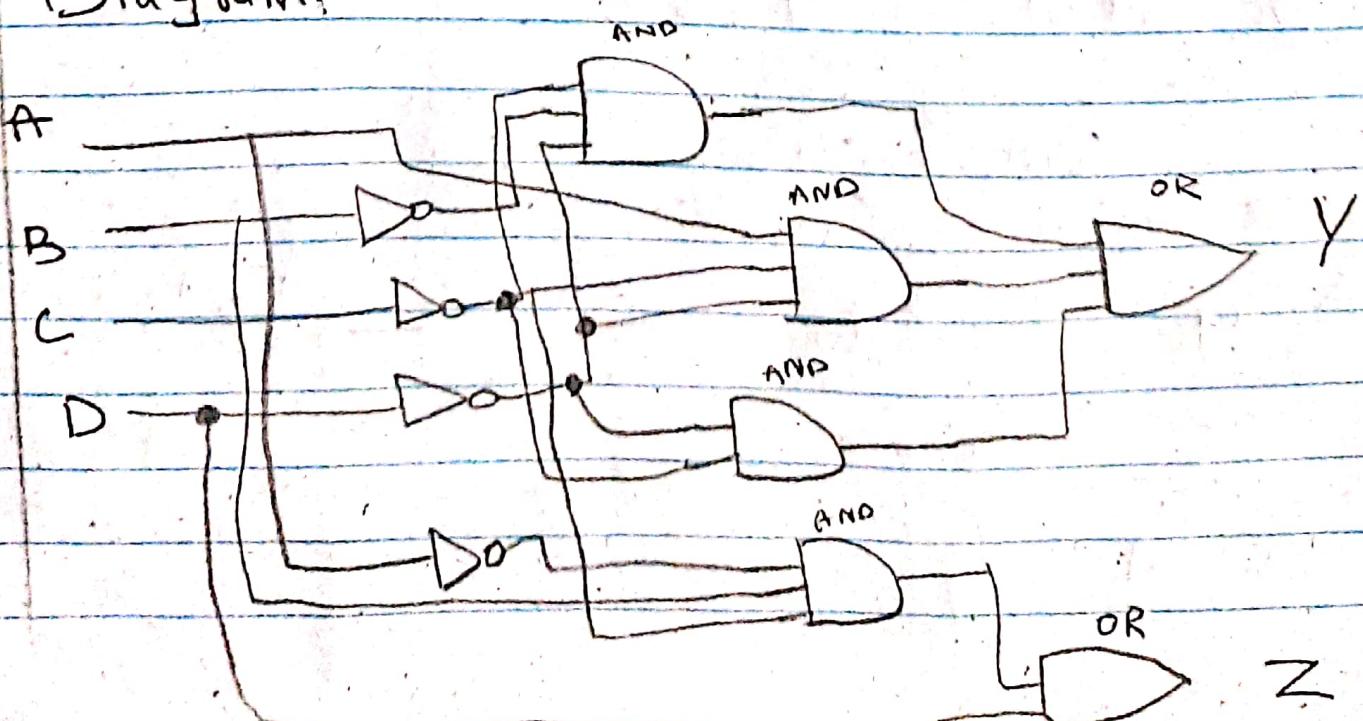

4) Given

$P = 0$ when $G = 1$ $S = 1$
 and $P = 0$ when $M = 0$ $S = 0$

| Logic 0 | Logic 1 | OR | P | Logic 0 | Logic 1 |
|---------|---------|----|---|---------|---------|
| 0 | 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 1 | 0 | 1 |
| 0 | 1 | 0 | 1 | 1 | 1 |
| 0 | 1 | 1 | 1 | 1 | 0 |
| 1 | 0 | 0 | 0 | 1 | 0 |
| 1 | 0 | 1 | 1 | 0 | 1 |
| 1 | 1 | 0 | 0 | 0 | 0 |
| 1 | 1 | 1 | 0 | 0 | 1 |

| BC | 00 | 01 | 11 | 10 |
|----------------|----|----|----|----|
| A ₀ | 0 | 0 | 1 | 1 |
| A ₁ | 1 | 0 | 0 | 0 |

$$(S+M) \cdot (\bar{G}+\bar{S})$$


For AND OR invert

$$(S+M) \cdot (\bar{G}+\bar{S})$$


$$\overline{(S+M)} + \overline{(\bar{G}+\bar{S})}$$

$$\bar{S}\bar{M} + GS$$

Diagram:

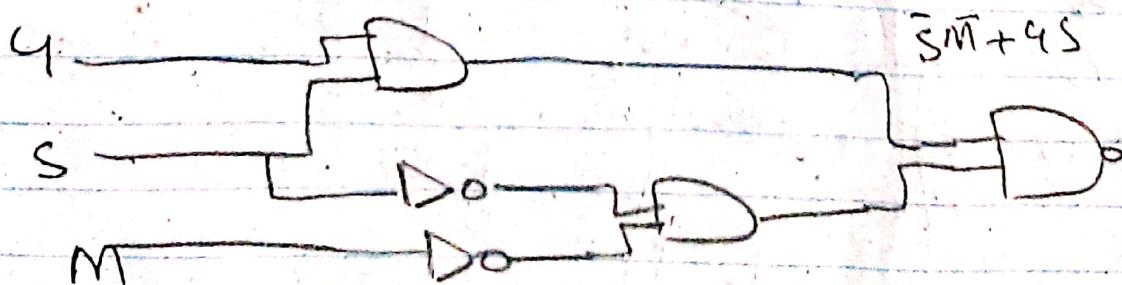

5)

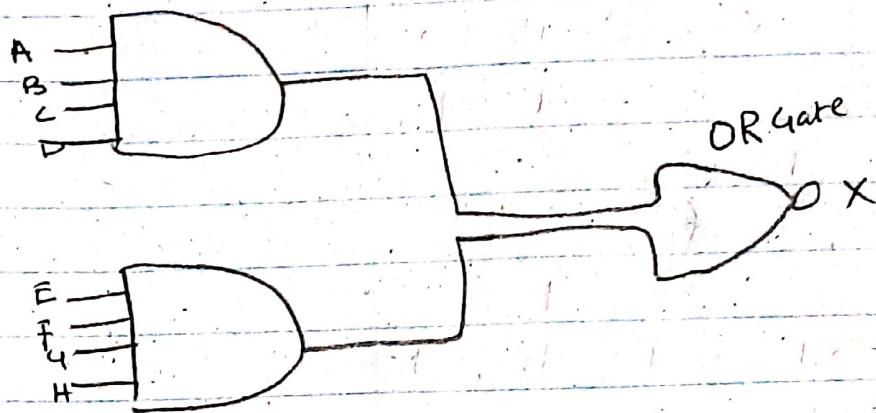

Boolean expression:

$$(ABCD) + (EFGH)$$

$$(ABCD) \cdot (EFGH)$$

$$(\bar{A} + \bar{B} + \bar{C} + \bar{D}) \cdot (\bar{E} + \bar{F} + \bar{G} + \bar{H})$$

Ans


6)

It is XOR gate.

| F switch | B switch | X |
|----------|----------|---|
| 0 | 0 | 0 |
| 0 | 1 | 1 |
| 1 | 0 | 1 |
| 1 | 1 | 0 |

Equation: $(A \oplus B) \text{ OR } (\bar{A}\bar{B} + A\bar{B})$

Diagram.

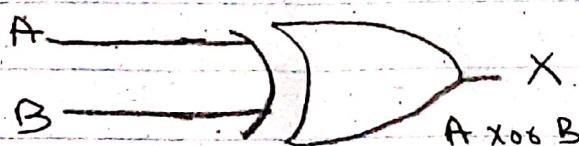

7)

Substituting values from given
Truth table

| | 00 | 01 | 11 | 10 |
|----|----|----|----|----|
| 00 | | | 1 | 1 |
| 01 | 1 | | | |
| 11 | | | | |
| 10 | 1 | 1 | 1 | 1 |

Simplified:

$$AB + ACD + \bar{A}\bar{B}C + \bar{A}B\bar{C}\bar{D}$$

Diagram:

